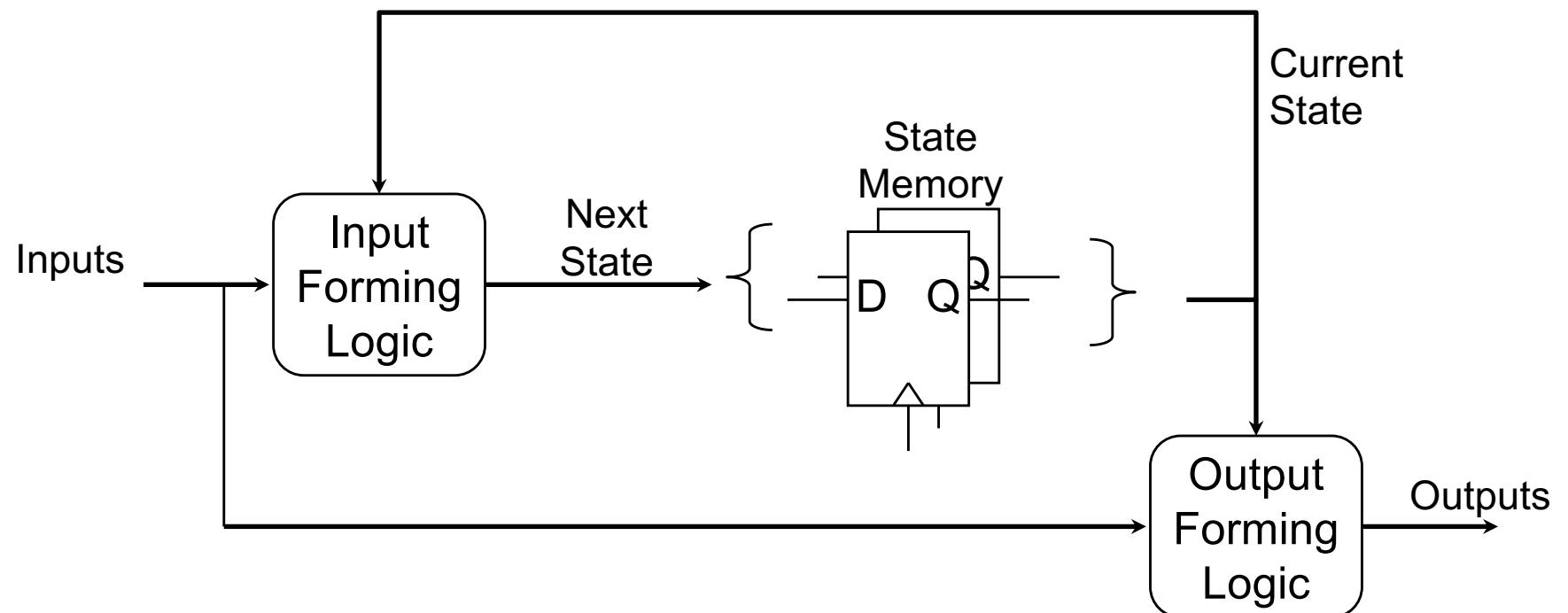


Register Transfer Level (RTL)

- Outputs are a function of current state and inputs




The always_ff Block

- Contains the input forming logic for the flip flops you are inferring.
- Uses a sensitivity list to describe when the flip flops load the new values
 - `always_ff @(posedge clock)`
 - Body of always block will not evaluate until a positive edge of the clock (positive edge FFs)
 - `always_ff @(negedge clock)`
 - Negative edge triggered flip-flops

Assignment Statements


- Use non-blocking assignment statements (`<=`)
- Flip-Flops will be inferred for all signals that are assigned within `always_ff` blocks
- Can use "if" and "case" statements
 - Do not need to cover all cases (memory element will hold previous value)

1-Bit Flip-Flop

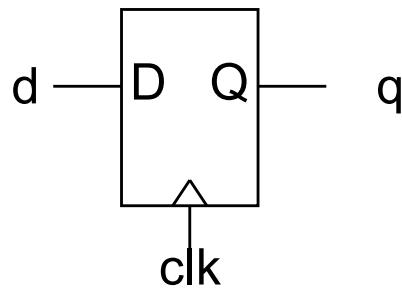

```
module ff(  
    input wire logic clk, d,  
    output logic q  
>;  
  
    always_ff @(posedge clk)  
        q <= d;  
  
endmodule
```

Loadable 1-Bit Flip-Flop

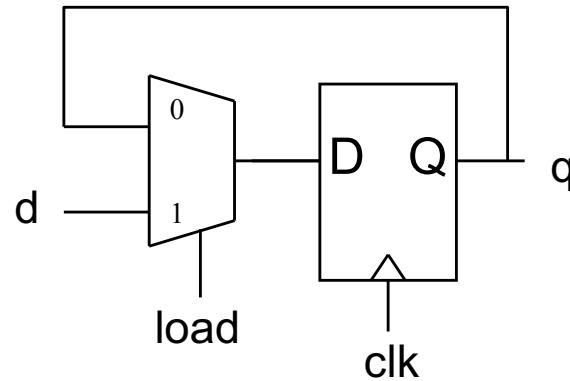

```
module ff(
    input wire logic clk, load, d,
    output logic q
);


    always_ff @(posedge clk)
        if (load)
            q <= d;

endmodule
```

if load is '1', load d to q
else nothing happens

Flip-Flops and Logic

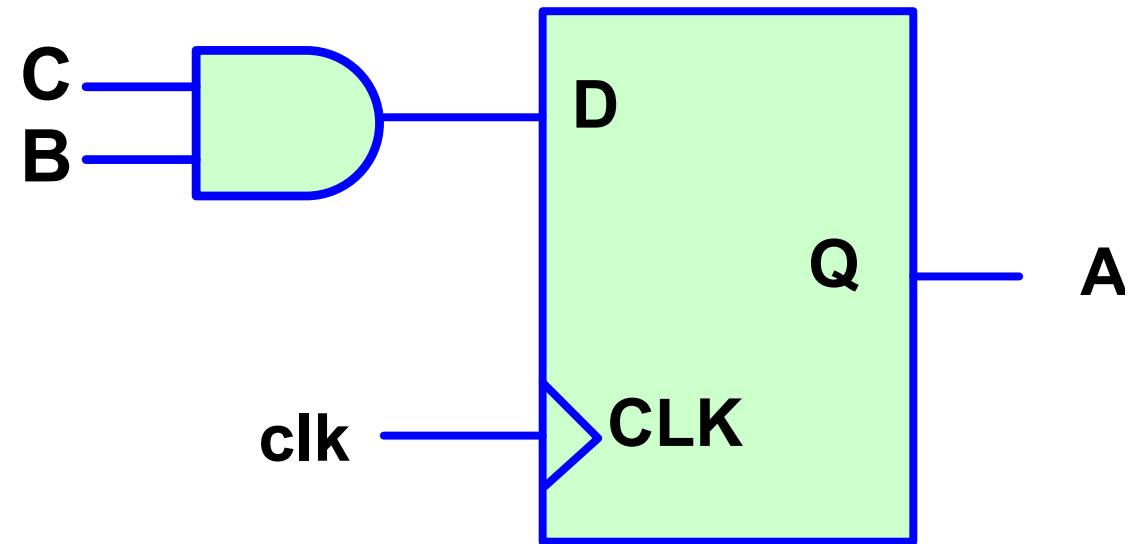
```
always_ff @ (posedge clk)
begin
    a <= b&c;
end
```



D Flip-Flop with Asynchronous Reset


```
always_ff @ (posedge clk  
          or negedge rst)  
begin  
    if (!rst) A <= 0;  
    else A <= B;  
end
```

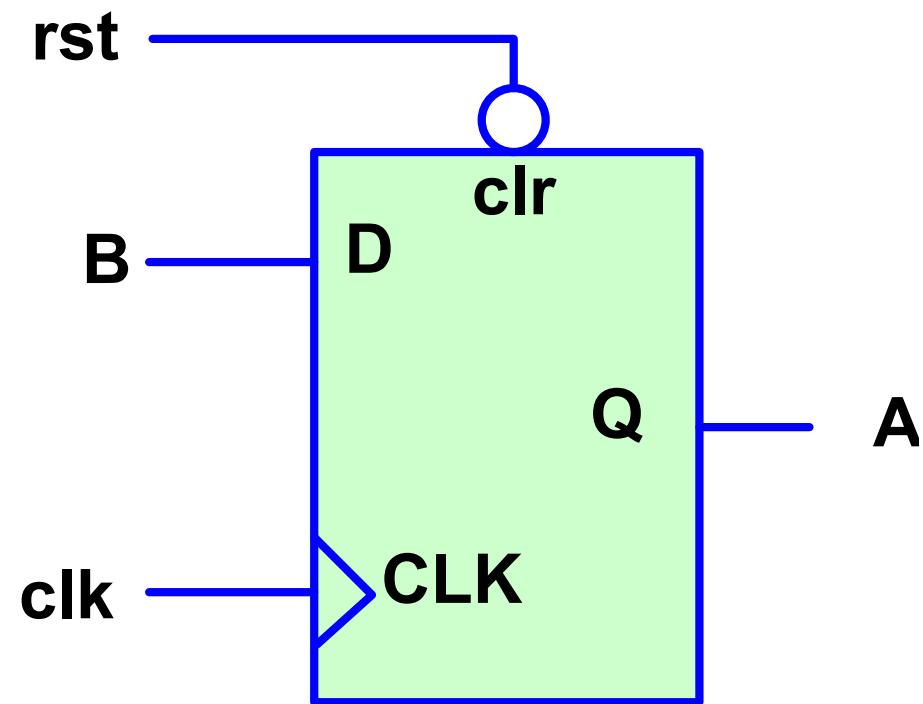To make the reset synchronous, just remove `negedge rst` from the sensitivity list.




D Flip-flop with Synchronous Reset and Enable
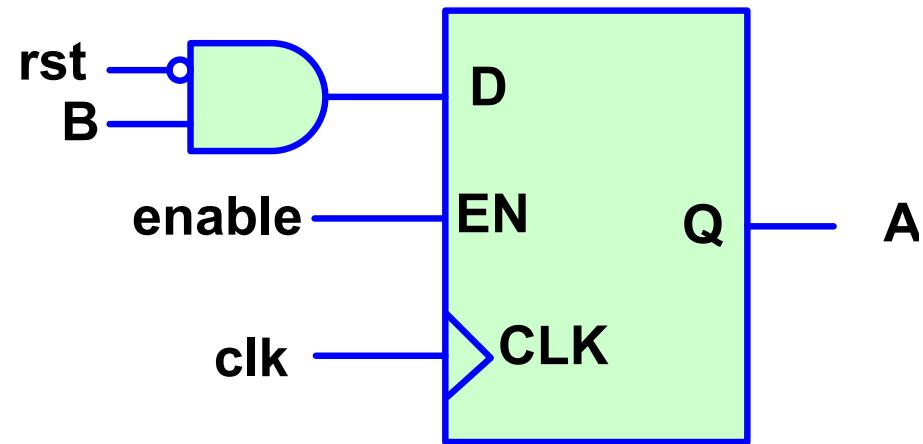
```
always_ff @ (posedge clk)
begin
    if (rst)
        A <= 0;
    else if (enable)
        A <= B;
end
```



A Parameterized Loadable Register

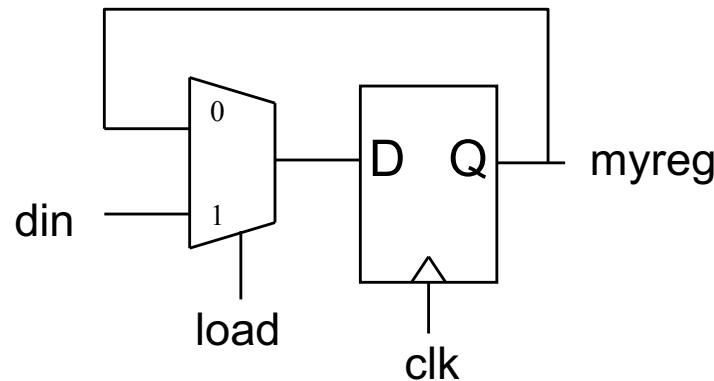

```
module LoadableReg #(WID=4) (
    input wire logic clk, load,
    input logic[WID-1:0] din,
    output logic[WID-1:0] myreg
);

    always_ff @ (posedge clk)
        if (load)
            myreg <= din;

endmodule
```


A Shift Register

```
logic[3:0] Q;  
always_ff @(posedge clk)  
begin  
    Q <= {Q[2:0],Q[3]}  
end
```




```
Q[3] <= Q[2];  
Q[2] <= Q[1];  
Q[1] <= Q[0];  
Q[0] <= Q[3];
```

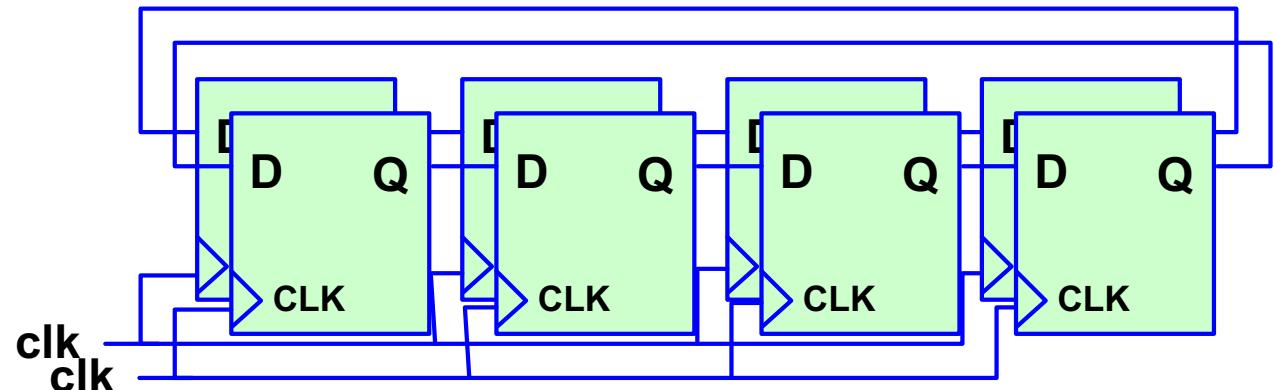Without a reset or load, this circuit can never be initialized.



A Parameterized Counter

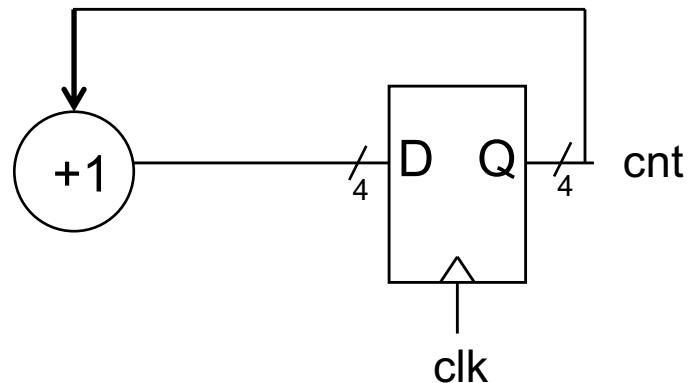


Without a clear or load, this circuit can never be initialized.

```
module upCnt #(WID=4)(  
    input wire logic clk,  
    output logic[WID-1:0] cnt  
);  
  
    always_ff @(posedge clk)  
        cnt <= cnt + 1;  
  
endmodule
```

Must have a clr signal to reset it to 0.
Otherwise, cnt would be in X state on startup.


A Counter with a Clear

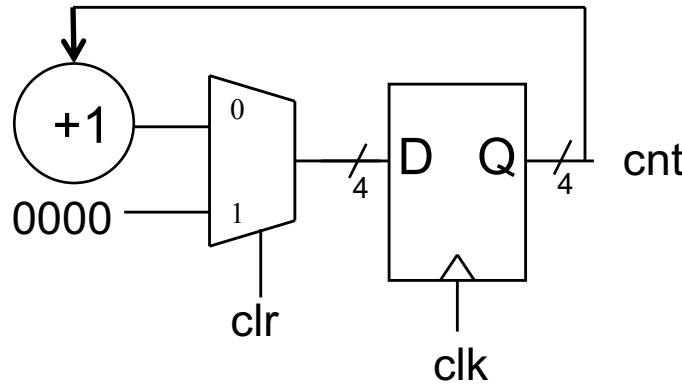

```
module upCnt #(WID=4)(  
    input wire logic clk, clr,  
    output logic[WID-1:0] cnt  
);  
  
    always_ff @ (posedge clk)  
        if (clr)  
            cnt <= 0;  
        else  
            cnt <= cnt + 1;  
endmodule
```

Must have a `clr` signal to reset it to 0.
Otherwise, `cnt` would be in X state on startup.


Current/Next State Values

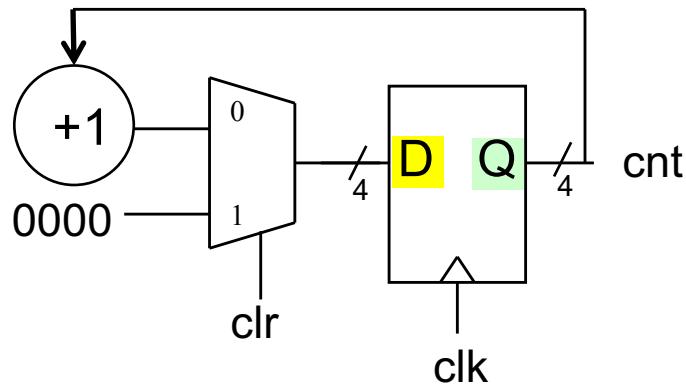


```
module upCnt #(WID=4)(  
    input wire logic clk, clr,  
    output logic[WID-1:0] cnt  
);  
  
    always_ff @ (posedge clk)  
        if (clr)  
            cnt <= 0;  
        else  
            cnt <= cnt + 1;  
endmodule
```

A Counter with Synchronous Reset and Enable
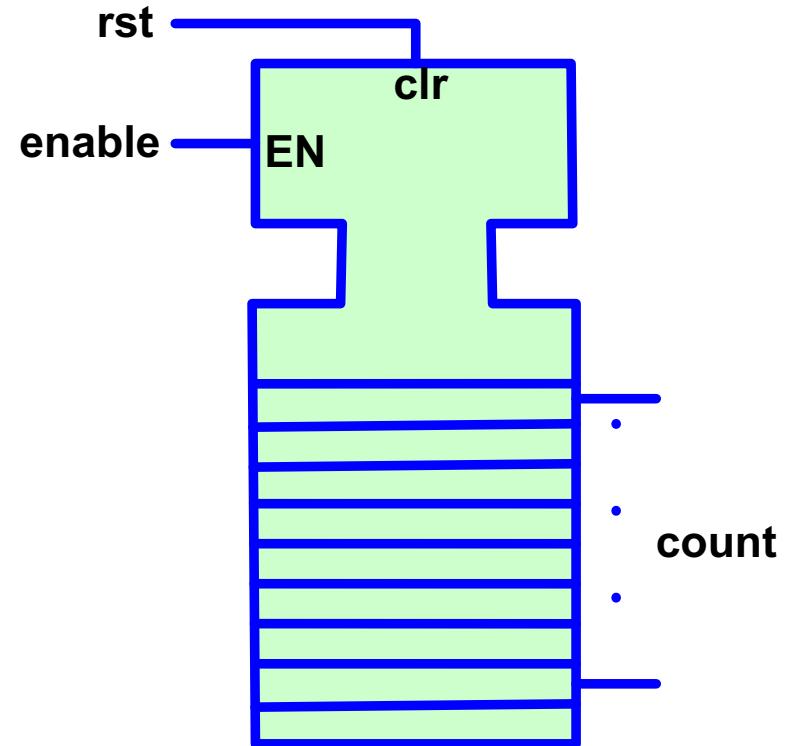
```
parameter WID=8;  
logic[WID-1:0] count;  
logic enable, reset;  
  
always_ff @(posedge clk)  
begin  
    if (reset)  
        count<=0;  
    else if (enable)  
        count<=count+1;  
end
```



Another Counter

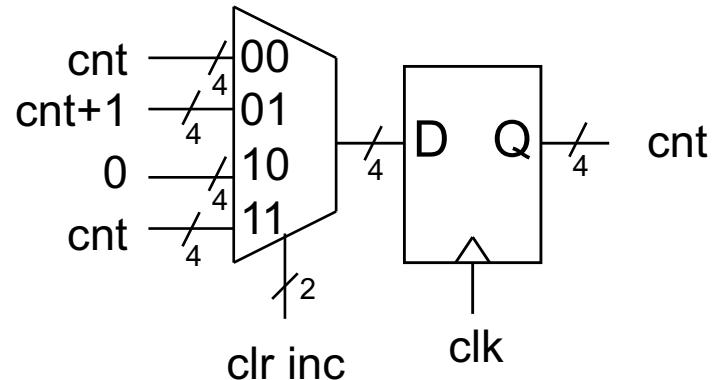


- A. `!clr && !inc`
- B. `!clr && inc`
- C. `clr && !inc`
- D. `clr && inc`

```
module upCnt #(WID=4) (
    input wire logic clk, clr, inc,
    output logic[WID-1:0] cnt
);


    always_ff @ (posedge clk)
        if (?)
            cnt <= 0;
        else if (?)
            cnt <= cnt + 1;
endmodule
```

Another Counter

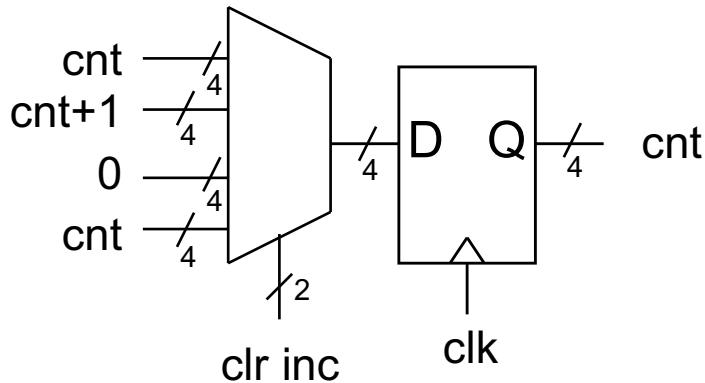

```
module upCnt #(WID=4)(  
    input wire logic clk, clr, inc,  
    output logic[WID-1:0] cnt  
);  
  
    always_ff @ (posedge clk)  
        if (clr && !inc)  
            cnt <= 0;  
        else if (!clr && inc)  
            cnt <= cnt + 1;  
endmodule
```

Yet Another Counter

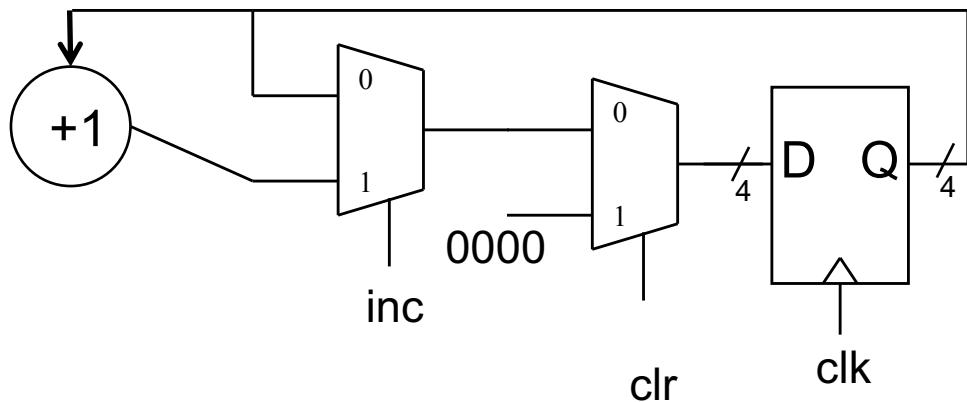


- A. `!clr`
- B. `clr`
- C. `!inc`
- D. `inc`

```
module upCnt #(WID=4) (
    input wire logic clk,
    input wire logic clr, inc,
    output logic[WID-1:0] q
);


    always_ff @ (posedge clk)
        if (?)
            q <= 0;
        else if (?)
            q <= q + 1;
endmodule
```

Yet Another Counter

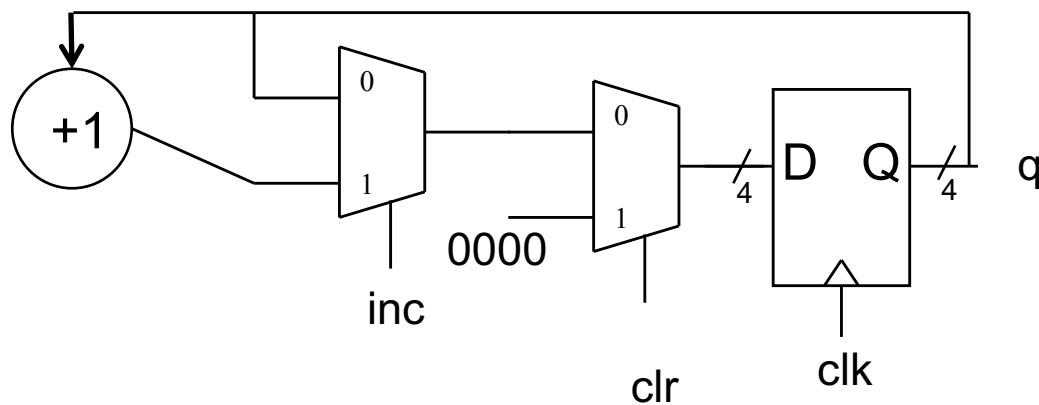

```
module upCnt #(WID=4)(  
    input wire logic clk,  
    input wire logic clr, inc,  
    output logic[WID-1:0] q  
);  
  
    always_ff @ (posedge clk)  
        if (clr)  
            q <= 0;  
        else if (inc)  
            q <= q + 1;  
endmodule
```

A Swapper

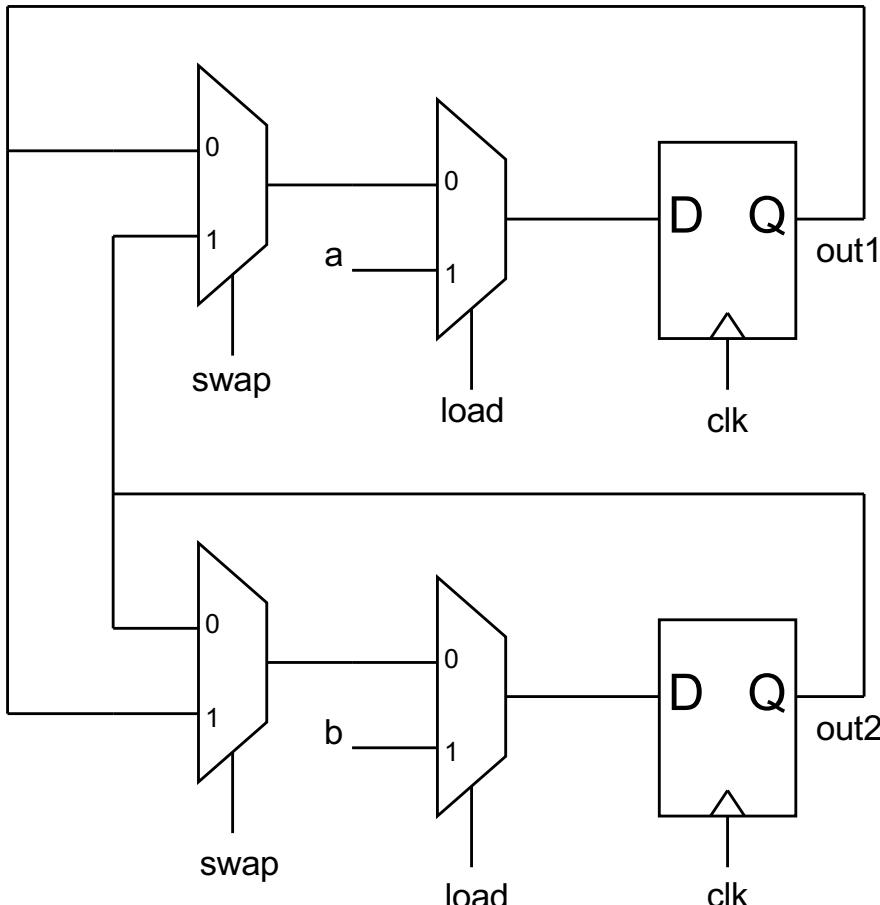


```
module swapper (
    input wire logic clk, load, swap,
    input wire logic a, b,
    output logic out1, out2
);

    always_ff @ (posedge clk)
        if (?)
            begin
                out1 <= a;
                out2 <= b;
            end
        else if (?)
            begin
                out1 <= out2;
                out2 <= out1;
            end
endmodule
```

- A. !load
- B. load
- C. !swap
- D. swap

A Swapper

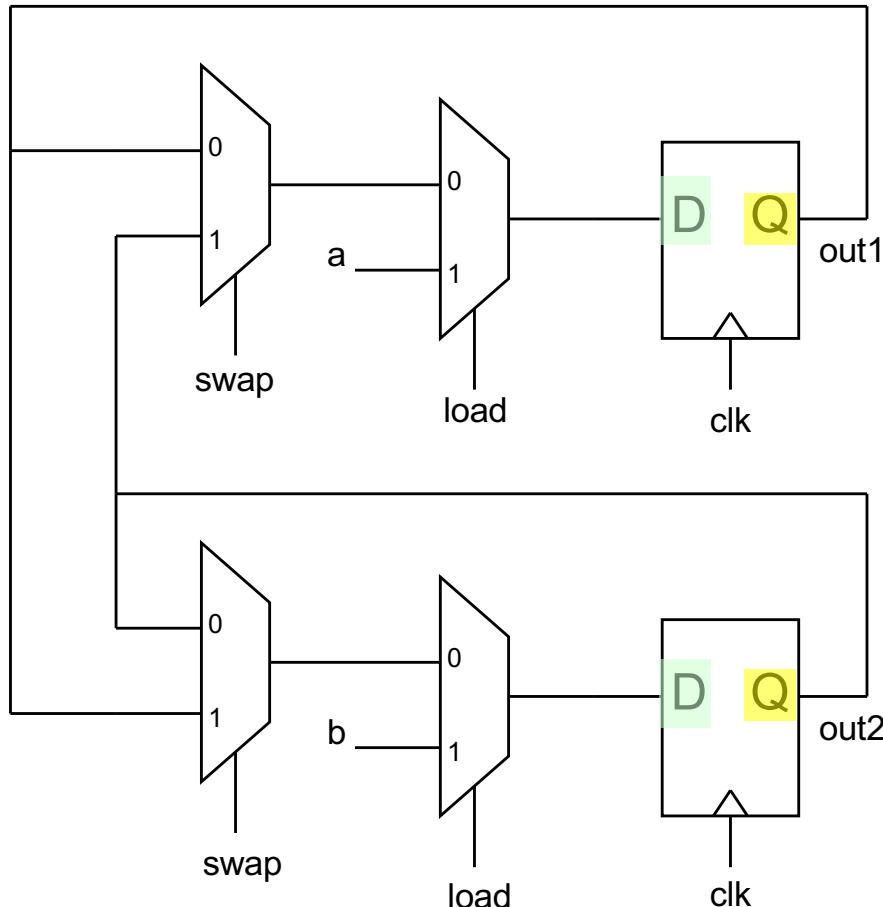


```
module swapper (
    input wire logic clk, load, swap,
    input wire logic a, b,
    output logic out1, out2
);

    always_ff @ (posedge clk)
        if (load)
            begin
                out1 <= a;
                out2 <= b;
            end
        else if (swap)
            begin
                out1 <= out2;
                out2 <= out1;
            end
endmodule
```

Multiple Assignments to a Signal

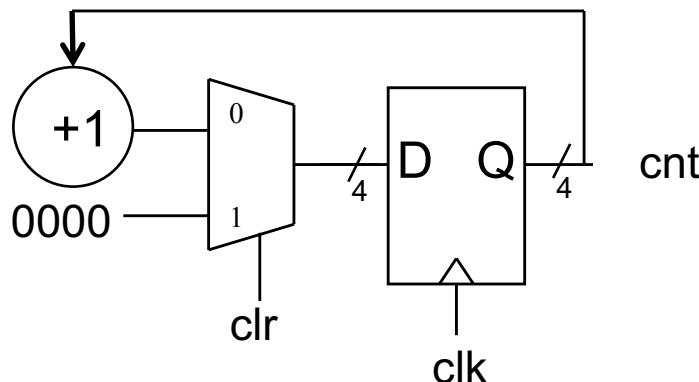
- When you assign twice...
 - Last one takes effect on the signal value



```
module multiAssign (
    input wire logic clk, clr,
    output logic[3:0] cnt
);

    always_ff @(posedge clk)
    begin
        cnt <= 4'b0000;
        if (!clr)
            cnt <= cnt+1;
    end
endmodule
```


A Shift Register

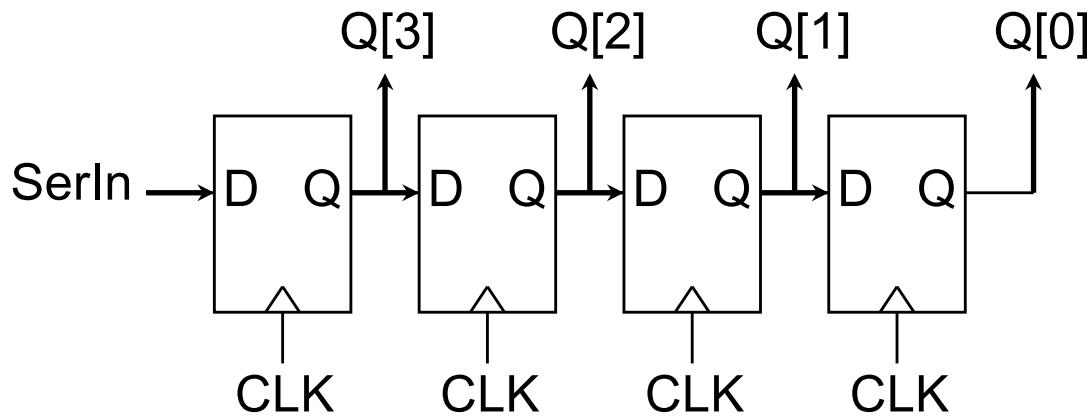

```
module delay4 (
    input wire logic clk, SerIn,
    output logic[3:0] Q
);
    always_ff @(posedge clk)
        Q <= ?;
endmodule
```

- A. {SerIn, Q[2:0]}
- B. {Q[3:1], SerIn}
- C. {SerIn, Q[3:1]}
- D. {Q[2:0], SerIn}
- E. {Q[2:1], SerIn}

A Shift Register

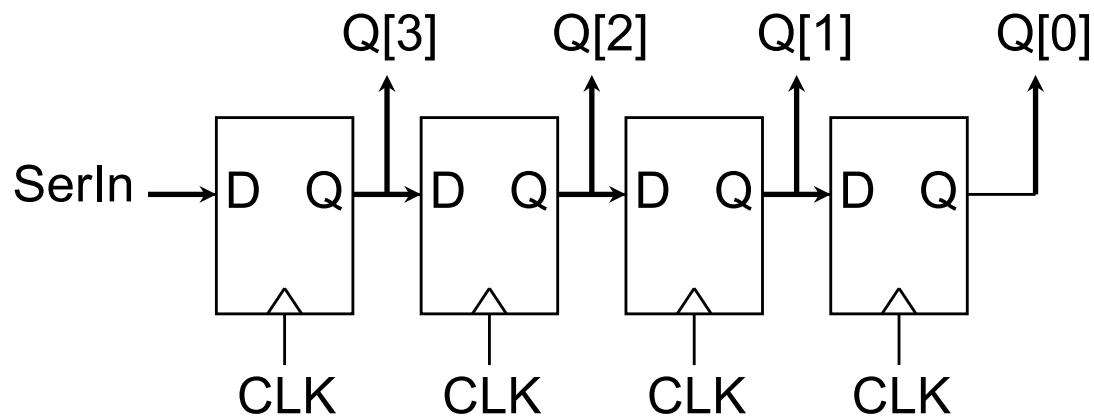


```
module delay4 (
    input wire logic clk, SerIn,
    output logic[3:0] Q
);

    always_ff @ (posedge clk)
        Q <= {SerIn, Q[3:1]};

endmodule
```


Another Shift Register

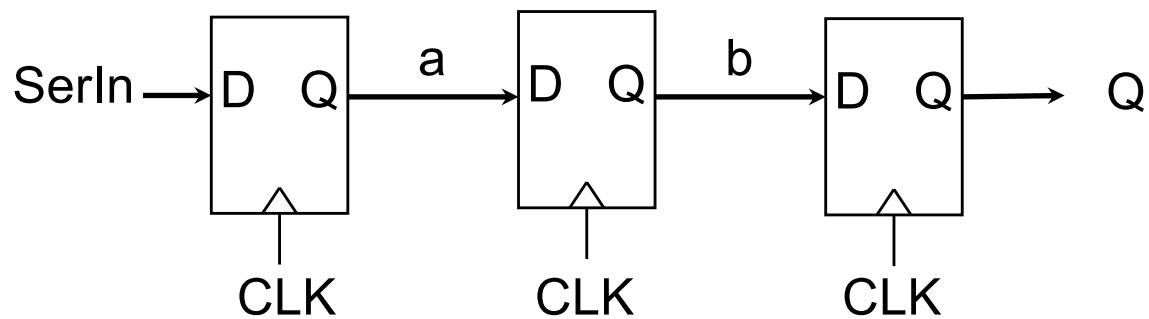

```
module delay3 (
    input wire logic clk,
    input wire logic SerIn,
    output logic Q
);
logic a, b;

always_ff @ (posedge clk)
begin
    a <= SerIn;
    b <= a;
    Q <= b;
end
endmodule
```

Yet Another Shift Register

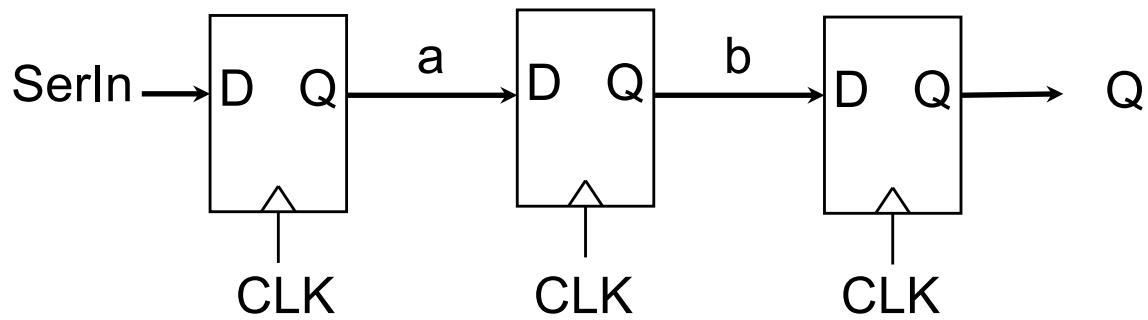


```
module delay3 (
    input wire logic clk,
    input wire logic SerIn,
    output logic Q
);
logic a, b;

always_ff @ (posedge clk)
begin
    Q <= b;
    b <= a;
    a <= SerIn;
end
endmodule
```

Order of assignments DOES NOT MATTER...

A Register File

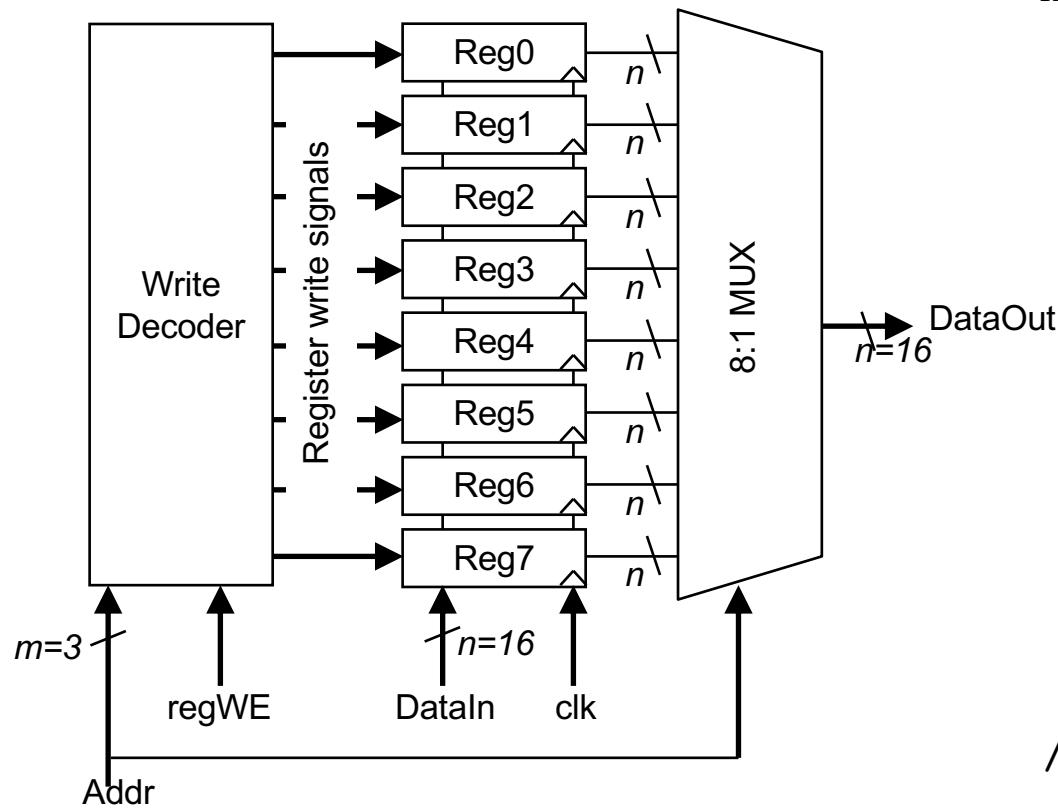

```
module regFile (
    input wire logic clk, regWE,
    input wire logic [2:0] Addr,
    input wire logic [15:0] DataIn,
    output logic[15:0] DataOut
);


logic [15:0] registers [8];

// The synchronous write logic
always_ff @ (posedge clk)
if (regWE)
    registers[Addr] <= ?;

// The asynchronous read logic
assign DataOut = ?;

endmodule
```

A Register File

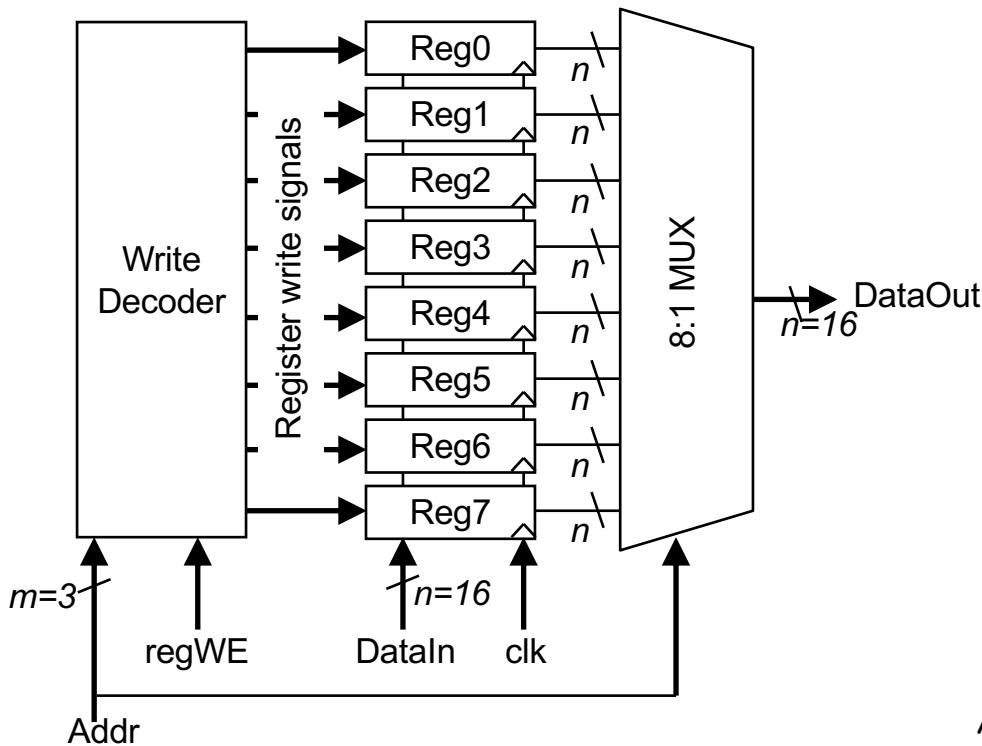

```
module regFile (
    input wire logic clk, regWE,
    input wire logic [2:0] Addr,
    input wire logic [15:0] DataIn,
    output logic[15:0] DataOut
);


logic [15:0] registers [8];

// The synchronous write logic
always_ff @(posedge clk)
if (regWE)
    registers[Addr] <= DataIn;

// The asynchronous read logic
assign DataOut = registers[Addr];

endmodule
```

A Register File

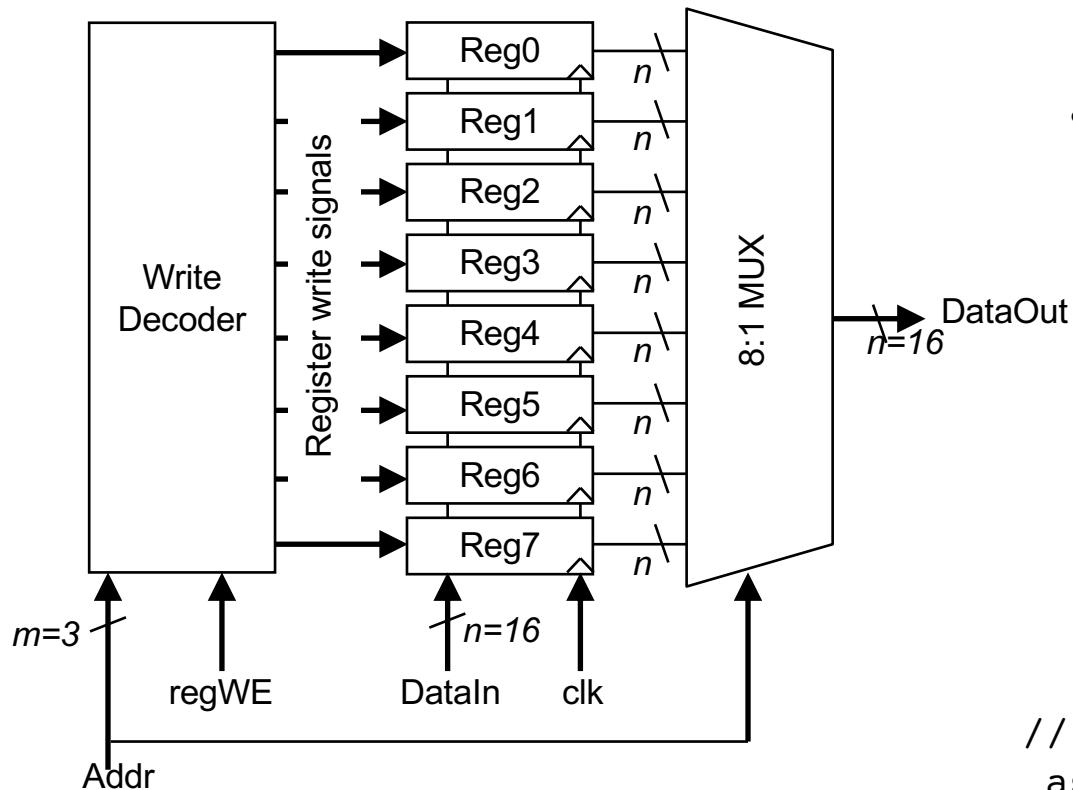

```
module regFile (
    input wire logic clk, regWE,
    input wire logic [2:0] Addr,
    input wire logic [15:0] DataIn,
    output logic[15:0] DataOut
);
    logic[15:0] Reg0,Reg1,Reg2,Reg3,
    Reg4,Reg5,Reg6,Reg7;
```

```
// The synchronous write logic
always_ff @(posedge clk)
if (regWE)
    case(Addr)
        3'b000: Reg0 <= DataIn;
        3'b001: Reg1 <= DataIn;
        3'b010: Reg2 <= DataIn;
        3'b011: Reg3 <= DataIn;
        3'b100: Reg4 <= DataIn;
        3'b101: Reg5 <= DataIn;
        3'b110: Reg6 <= DataIn;
        default: Reg7 <= DataIn;
    endcase

// The asynchronous read logic
assign DataOut = (Addr==3'000)? Reg0:
    (Addr==3'001)? Reg1:
    ..... .
    reg7;

endmodule
```